

EE-2007 52-68

AI24BTECH11012- Pushkar Gudla

- 1) The integral $\frac{1}{2\pi} \int_0^{2\pi} \sin(t - \tau) \cos \tau, d\tau$ equals:
- $\sin t \cos t$
 - 0
 - $\frac{1}{2} \cos t$
 - $\frac{1}{2} \sin t$
- 2) $X(z) = 1 - 3z^{-1}$, $Y(z) = 1 + 2z^{-2}$ are Z-transforms of two signals $x[n], y[n]$ respectively. A linear time invariant system has the impulse response $h[n]$ defined by these two signals as:

$$h[n] = x[n - 1] * y[n]$$

where $*$ denotes discrete time convolution. Then the output of the system for the input $\delta[n - 1]$ is:

- Has Z-transform $z^{-1}X(z)Y(z)$
 - Equals $\delta[n - 2] - 3\delta[n - 3] + 2\delta[n - 4] - 6\delta[n - 5]$
 - Has Z-transform $1 - 3z^{-1} + 2z^{-2} - 6z^{-3}$
 - Does not satisfy any of the above three
- 3) A loaded dice has the following probability distribution of occurrences:

Dice value	1	2	3	4	5	6
Probability	$\frac{1}{4}$	$\frac{1}{8}$	$\frac{1}{8}$	$\frac{1}{8}$	$\frac{1}{8}$	$\frac{1}{4}$

If three identical dice as the above are thrown, the probability of occurrence of values 1, 5, and 6 on the three dice is:

- Same as that of occurrence of 3, 4, 5
 - Same as that of occurrence of 1, 2, 5
 - $\frac{1}{128}$
 - $\frac{5}{8}$
- 4) Let x and y be two vectors in a 3-dimensional space and $\langle x, y \rangle$ denote their dot product. Then the determinant

$$\det \begin{bmatrix} \langle x, x \rangle & \langle x, y \rangle \\ \langle y, x \rangle & \langle y, y \rangle \end{bmatrix}$$

- is zero when x and y are linearly independent
 - is positive when x and y are linearly independent
 - is non-zero for all non-zero x and y
 - is zero only when either x or y is zero
- 5) The linear operation $L(x)$ is defined by the cross product $L(x) = \mathbf{b} \times x$, where $\mathbf{b} = [0, 1, 0]^T$ and $x = [x_1, x_2, x_3]^T$ are three-dimensional vectors. The 3×3 matrix \mathbf{M} of this operation satisfies:


$$L(x) = \mathbf{M} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}$$

Then the eigenvalues of \mathbf{M} are:

- 0, +1, -1


- b) $1, -1, 1$
- c) $i, -i, 1$
- d) $i, -i, 0$

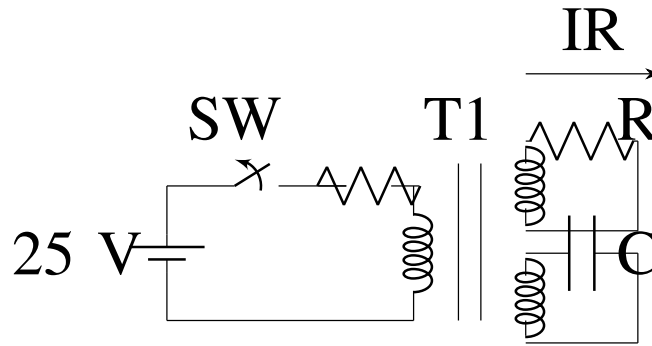
6) In the figure, transformer T_1 has two secondaries all three windings having the same number of turns and with polarities as indicated. One secondary is shorted by a 10Ω resistor R , and the other by a $15\mu F$ capacitor. The switch SW is opened ($t = 0$) when the capacitor is charged to $5V$ with the left plate as positive. At $t = 0+$ the voltage V_p and current I_R are




- a) $-25V, 0.0A$
- b) very large voltage, very large current
- c) $5.0V, 0.5A$
- d) $-5.0V, -5.0A$

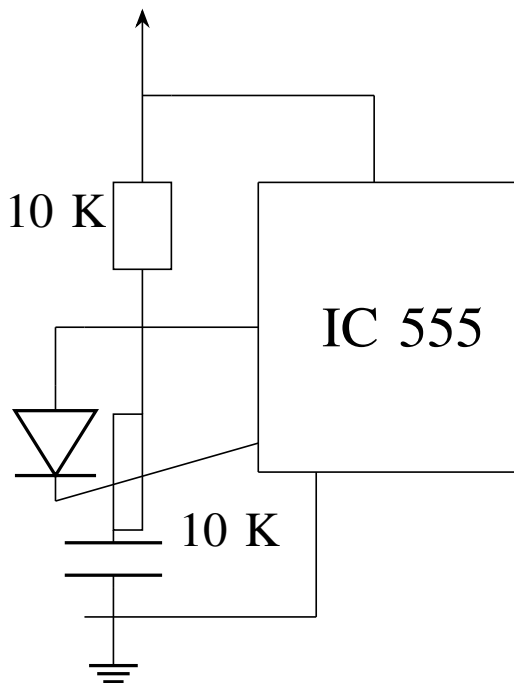7) IC 555 in the adjacent figure is configured as an astable multivibrator. it is enabled to oscillate at $t = 0$ by applying a high input to pin 4. The pin description is: 1 and 8-supply; 2-trigger; 4-reset; 6-threshold; 7-discharge. The waveform appearing across the capacitor starting from $t = 0$, as observed on a storage CRO is:



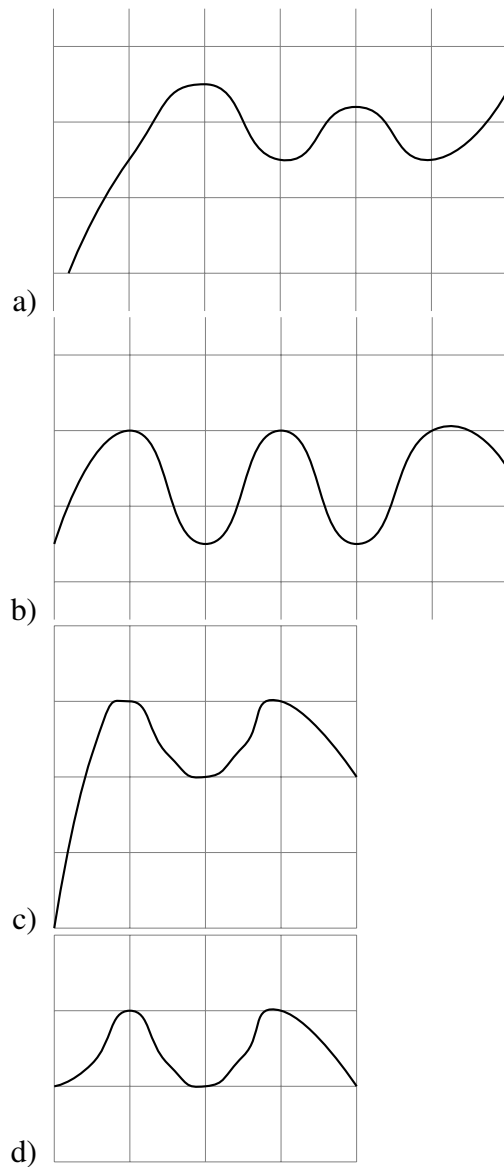

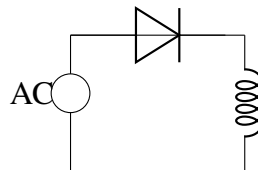
8) In the circuit figure the diode connects the ac source to a pure inductance L . The diode conducts for




- a) 90°
- b) 180°
- c) 270°
- d) 360°

9) The circuit in the figure is a current commutated dc-dc chopper where, Th_M is the main SCR and Th_{AUX} is the auxiliary SCR. The load current is constant at 10 A. Th_M is turned OFF between


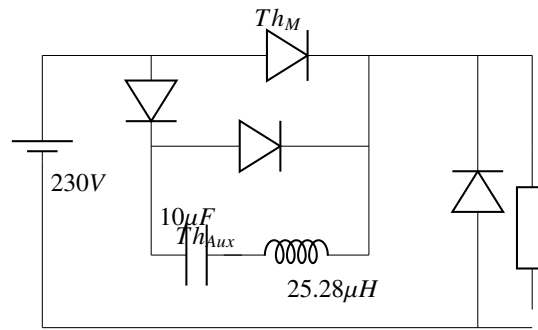
- a) $0\mu s < t \leq 25\mu s$
- b) $25\mu s < t \leq 50\mu s$
- c) $50\mu s < t \leq 75\mu s$
- d) $75\mu s < t \leq 100\mu s$




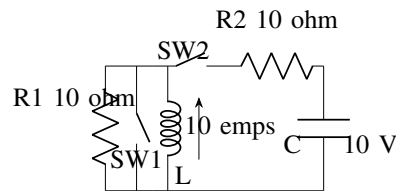- 10) In the circuit shown in figure switch SW_1 is initially CLOSED and SW_2 is OPEN. The inductor L carries a current of 10 A and the capacitor is charged to 10 V with polarities as indicated. SW_2 is initially CLOSED at $t = 0^-$ and SW_1 is OPENED at $t = 0$. The current through C and the voltage across L at $t = 0^+$ is




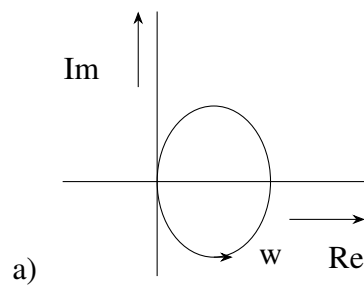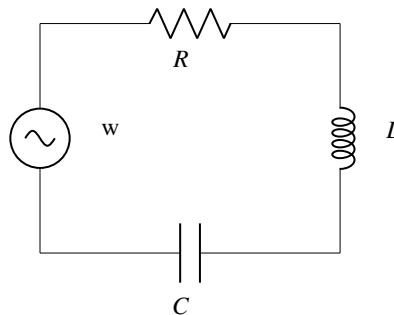
- a) 55A, 4.5V
 b) 5.5A, 45V
 c) 45A, 5.5V
 d) 4.5A, 55V
- 11) The R-L-C series circuit shown is supplied from a variable frequency voltage source. The admittance-locus of the R-L-C network at terminals AB for increasing frequency ω is



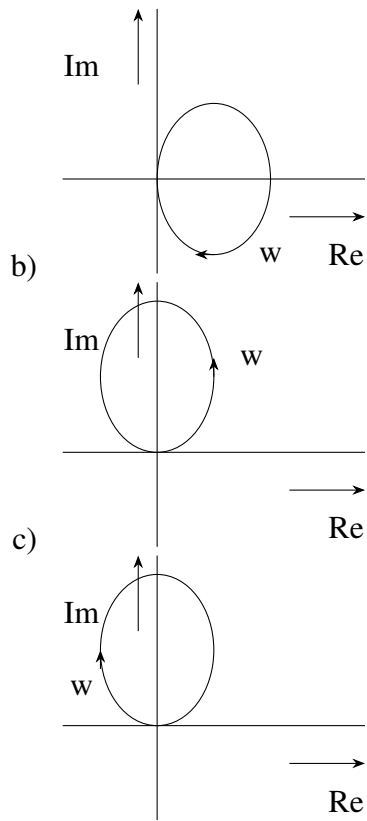


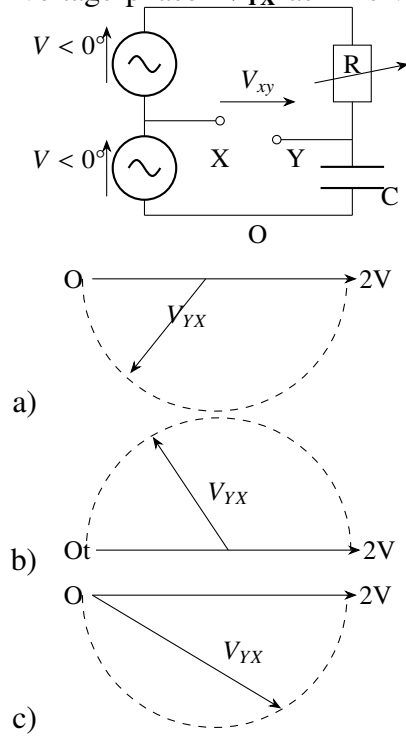- 12) In the figure given below all phasors are with reference to the potential at point "O". The locus of voltage phasor V_{YX} as R is varied from zero to infinity is shown by



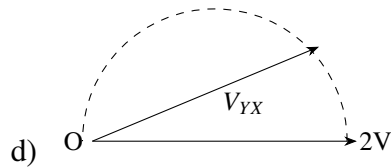

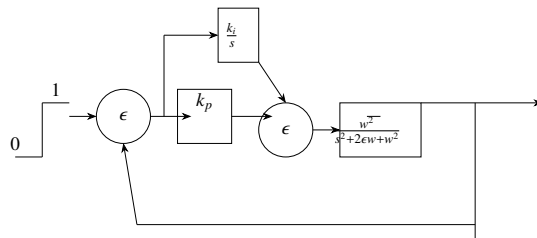- 13) A 3 V dc supply with an internal resistance of 2Ω supplies a passive non-linear resistance characterized by the relation $V_{NL} = I_{NL}^2$. The power dissipated in the non-linear resistance is
- 1.0W
 - 1.5W
 - 2.5W
 - 3.0W
- 14) Consider the feedback control system shown below which is subjected to a unit step input. The system is stable and has the following parameters $k_p = 4$, $K_1 = 10$, $w = 500$ and $\epsilon = 0.7$. The steady state value of z is.



- 1
 - 0.25
 - 0.1
 - 0
- 15) A three-phase squirrel cage induction motor has a starting torque of 150% and a maximum torque of 300% with respect to rated torque at rated voltage and rated frequency. Neglect the stator resistance and rotational losses. The value of slip for maximum torque is \hat{A}
- 13.48%
 - 16.24%
 - 18.92%
 - 26.79%
- 16) The matrix A given below is the node incidence matrix of a network. The columns correspond to branches of the network while the rows correspond to nodes. Let $V = [v_1 \ v_2 \ \dots v_6]^T$ denote the vector of branch voltages while $I = [i_1 i_2 \dots i_6]^T$ that of branch currents. The vector $E = [e_1 \ e_2 \ e_3 \ e_4]^T$ denotes the vector of node voltages relative to a common ground. \hat{A}

$$A = \begin{bmatrix} 1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 0 & -1 & -1 \\ 0 & 0 & -1 & 1 & 0 & 1 \end{bmatrix}$$

Which of the following statements is true?

- The equations $v_1 - v_2 + v_3 = 0$, $v_3 + v_4 - v_5 = 0$ are KVL equations for the network for some loops
 - The equations $v_1 - v_3 - v_6 = 0$, $v_4 + v_5 - v_6 = 0$ are KVL equations for the network for some loops
 - $E = AV$
 - $AV = 0$ are KVL equations for the network
- 17) An isolated 50 Hz synchronous generator is rated at 15MW, which is also the maximum continuous power limit of its prime mover. It is equipped with a speed governor with 5% droop. Initially, the

generator is feeding three loads of $4MW$ each at 50 Hz . One of these loads is programmed to trip permanently if the frequency falls below $48Hz$. If an additional load of $3.5MW$ is connected, then the frequency will settle down to \hat{A}

- a) $49.417Hz$
- b) $49.917Hz$
- c) $50.083Hz$
- d) $50.583Hz$