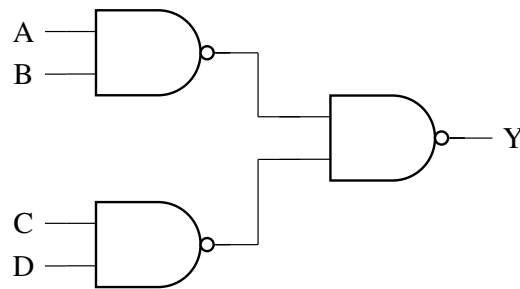


AE-2015 14-26


AI24BTECH11012- Pushkar Gudla

1) In the logic circuit shown in the figure, Y is given by



- a) $Y=ABCD$
- b) $Y=(A+B)(C+D)$
- c) $Y=A+B+C+D$
- d) $Y=AB+CD$

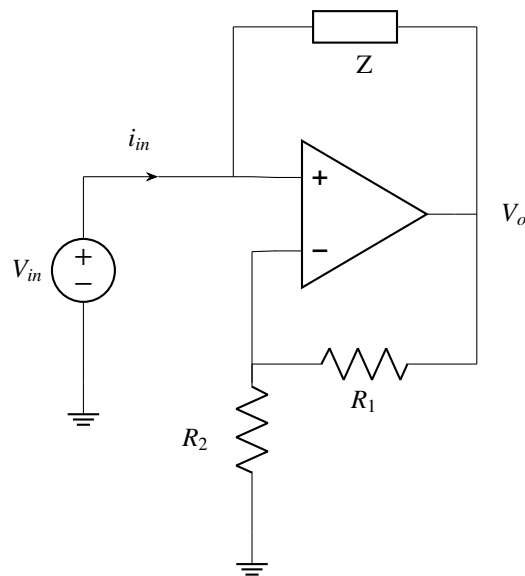2) The op-amp shown in the figure is ideal. The input impedance $\frac{v_{in}}{i_{in}}$ is given by




- a) $Z \frac{R_1}{R_2}$
- b) $-Z \frac{R_2}{R_1}$
- c) Z
- d) $-Z \frac{R_1}{R_1+R_2}$


3) A continuous-time input signal $x(t)$ is an eigenfunction of an LTI system, if the output is

- a) $kx(t)$, where k is an eigenvalue
- b) $ke^{i\omega t}x(t)$ where k is an eigenvalue and $e^{i\omega t}$ is a complex exponential signal
- c) $x(t)e^{i\omega t}$, where $e^{i\omega t}$ is a complex signal
- d) $kH(\omega)$, where k is an eigenvalue and $H(\omega)$ is a frequency response of the system

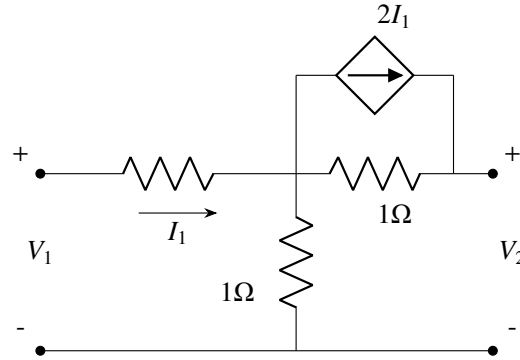- 4) Consider a non-singular 2×2 square matrix \mathbf{A} . If $\text{trace}(\mathbf{A}) = 4$ and $\text{trace}(\mathbf{A}^2) = 5$, the determinant of the matrix \mathbf{A} is _____(up to 1 decimal place).
- 5) Let f be a real-valued function of a real variable defined as $f(x) = x - [x]$, where $[x]$ denoted the largest integer less than or equal to x . The value of $\int_{0.25}^{1.25} f(x)dx$ is _____(up to 2 decimal places).
- 6) In the two-port network shown, the h_{11} parameter (where, $h_{11} = \frac{V_1}{I_1}$, when $V_2 = 0$ in ohms is _____(up to 2 decimal places).



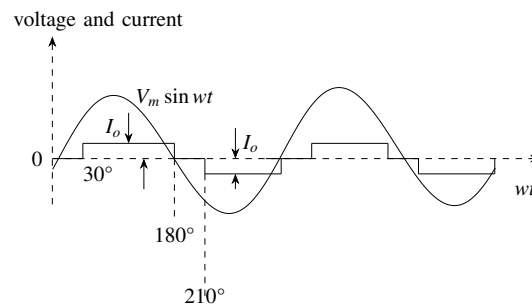- 7) The series impedance matrix of a short three-phase transmission line in phase coordinates $\begin{bmatrix} Z_s & Z_m & Z_m \\ Z_m & Z_s & Z_m \\ Z_m & Z_m & Z_s \end{bmatrix}$ is given. If the positive sequence impedance is $(1 + j10)\Omega$, and the zero sequence impedance is $(4 + j31)\Omega$, then the imaginary part of Z_m (in Ω) is _____ (up to 2 decimal places).
- 8) The positive, negative and zero sequence impedances of a 125 MVA, three-phase, 15.5 kV, star-grounded, 50 Hz generator are $j0.1$ pu, $j0.05$ pu, and $j0.01$ pu respectively on the machine rating base. The machine is unloaded and working at the rated terminal voltage. If the grounding impedance of the generator is $j0.01$ pu, then the magnitude of fault current for a b -phase to ground fault (in kA) is _____ (up to 2 decimal places).
- 9) A 1000×1000 bus admittance matrix for an electric power system has 8000 non-zero elements. The minimum number of branches (transmission lines and transformers) in this system are _____(up to 2 decimal places).
- 10) The waveform of the current drawn by a semi-converter from a sinusoidal AC voltage source is shown in the figure. If $I_o = 20$ A, the rms value of fundamental component of the current is _____A(up to 2 decimal places).




- 11) A separately excited dc motor has an armature resistance $R_a = 0.05\Omega$. The field excitation is kept constant. At an armature voltage of 100V, the motor produces a torque of 500 Nm at zero speed. Neglecting all mechanical losses, the no-load speed of the motor(in radian/s) for an armature voltage of 150 V is _____(up to 2 decimal places).

- 12) Consider a unity feedback system with forward transfer function given by

$$G(s) = \frac{1}{(s+1)(s+2)}$$

The steady-state error in the output of the system for a unit-step input is _____ (up to 2 decimal places).

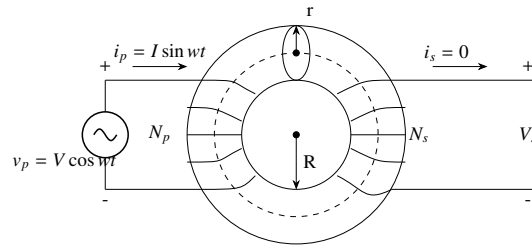- 13) A transformer with toroidal core of permeability μ is shown in the figure. Assuming uniform flux density across the circular core cross-section of radius $r < R$, and neglecting any leakage flux, the best estimate for the mean radius R is



- a) $\frac{\mu V r^2 N_p^2 w}{I}$
b) $\frac{\mu I r^2 N_p N_s w}{V}$
c) $\frac{\mu V r^2 N_p^2 w}{2I}$
d) $\frac{\mu I r^2 N_p^2 w}{2V}$